

$$I = \frac{V}{R + j\omega L + \frac{1}{j\omega C}}$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega_0^2 = \frac{1}{LC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

(1)

$$I = \frac{|V|}{R}$$

$$\varphi = \sum_i \varphi_{zi} - \sum_i \varphi_{pi} = k\pi$$

$$R + sL + \frac{1}{sC} = 0 \quad s^2 LC + sRC + 1 = 0$$

$$s = \frac{-RC \pm \sqrt{R^2 C^2 - 4LC}}{2LC} = -\frac{R}{2L} \pm \frac{R}{2L} \sqrt{1 - \frac{4L^2}{R^2 C^2}}$$


$$s^2 + s \frac{R}{L} + \frac{1}{LC} = 0$$

$$s_{1,2} = -\frac{R}{2L} \pm \frac{1}{2} \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}} = -\frac{R}{2L} \pm j \sqrt{\frac{1}{LC} - \frac{1}{4} \left(\frac{R}{L}\right)^2}$$

$$s_{1,2} = -\frac{R}{2L} \pm j\omega_0 \sqrt{1 - \frac{1}{4} \left(\frac{R}{2\omega_0 L}\right)^2} \quad Q = \frac{L\omega_0}{R}$$

$$s_{1,2} = -\frac{R}{2L} \pm j\omega_0 \sqrt{1 - \frac{1}{4Q^2}} \quad Q \gg 1$$
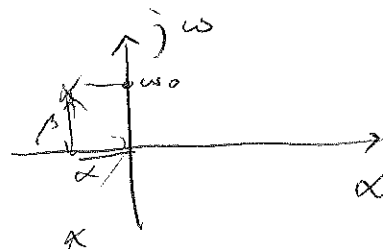
$$s_{1,2} = -\underbrace{\frac{R}{2L}}_{\alpha} \pm j \underbrace{\omega_0}_{\beta} \quad \frac{\beta}{2\alpha} = \frac{\omega_0 L}{R} = Q$$



$$I = \frac{V}{\sqrt{R^2 + \omega^2 L^2}}$$

$$I = \frac{V}{\sqrt{R^2 + \omega^2 \left(1 - \frac{1}{\omega^2 C^2}\right)^2}}$$

(2)

$$= \frac{V}{\sqrt{R^2 + \omega^2 L^2 \left(1 - \frac{\omega_0^2}{\omega^2}\right)^2}} = \frac{V}{R \sqrt{1 + \frac{\omega^2 L^2}{R^2} \left(1 - \frac{\omega_0^2}{\omega^2}\right)^2}}$$

$$2 = 1 + \frac{\omega_{dB}^2 L^2}{R^2} \left(1 - \frac{\omega_0^2}{\omega_{dB}^2}\right)^2$$

$$\left(1 - \frac{\omega_0^2}{\omega_{-3dB}^2}\right)^2 = \frac{R^2}{\omega_{-3dB}^2 L^2}$$

$$\frac{(\omega_{-3dB}^2 - \omega_0^2)}{\omega_{-3dB}^2} = \frac{R}{\omega_{-3dB} L}$$


$$\frac{(\omega_{-3dB} + \omega_0)(\omega_{-3dB} - \omega_0)}{\omega_{-3dB}^2} = \frac{R}{\omega_{-3dB} L}$$

$$\frac{2 \omega_0 (\omega_{-3dB} - \omega_0)}{\omega_0^2} = \frac{R}{\omega_0 L}$$

$$2(\omega_{-3dB} - \omega_0) = BW = \frac{R}{\omega_0 L}$$

$$\frac{BW}{\omega_0} = \frac{R}{\omega_0 L} = \frac{1}{Q} \quad \frac{BW}{\omega_0} = \frac{1}{Q}$$

(3)

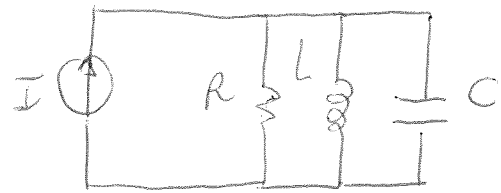

$$V = \frac{I}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C}$$

$$\omega_0 \quad \omega_0^2 = \frac{1}{LC} \quad |V| = |I|/R$$

$$\frac{1}{R} + \frac{1}{j\omega L} + j\omega C = 0 \quad \omega^2 LCR + R + j\omega L = 0$$

L

$$\omega^2 LC + 0 \frac{L}{R} + 1 = 0$$

$$\omega_{1,2} = -\frac{1}{2RC} \pm \frac{1}{2LC} \sqrt{\left(\frac{L}{R}\right)^2 - 4LC}$$

$$= -\frac{1}{2RC} \pm j \frac{1}{2LC} \sqrt{4LC - \left(\frac{L}{R}\right)^2}$$

$$L = \frac{1}{\omega_0^2 C}$$

$$= -\frac{1}{2RC} \pm j \frac{2}{2LC} \sqrt{LC - \frac{1}{4} \left(\frac{L}{R}\right)^2} = -\frac{1}{2RC} \pm j \frac{\sqrt{LC}}{LC} \sqrt{1 - \frac{1}{4} \left(\frac{\sqrt{LC}}{RC \sqrt{LC}}\right)^2}$$

$$= -\frac{1}{2RC} \pm j \frac{1}{LC} \sqrt{LC \left(1 - \frac{1}{4} \frac{LC}{\omega_0^2 R^2}\right)}$$

$$= -\frac{1}{2RC} \pm j \frac{1}{LC} \sqrt{LC \left(1 - \frac{1}{4LC} \left(\frac{L}{R}\right)^2\right)} = -\frac{1}{2RC} \pm j \frac{\sqrt{LC}}{LC} \sqrt{1 - \frac{1}{4} \frac{L}{CR^2}}$$


$$= -\frac{1}{2RC} \pm j \omega_0 \sqrt{1 - \frac{1}{4} \frac{1}{\omega_0^2 C^2 R^2}} \quad Q = \omega_0 CR$$

$$= -\frac{1}{2RC} \pm j \omega_0 \sqrt{1 - \frac{1}{4Q^2}} = -\frac{1}{2RC} \pm j \omega_0 \quad \beta = \omega_0$$

$$2\alpha = \frac{1}{RC}$$

$$\frac{\beta}{2\alpha} = \omega_0 RC = Q$$

④

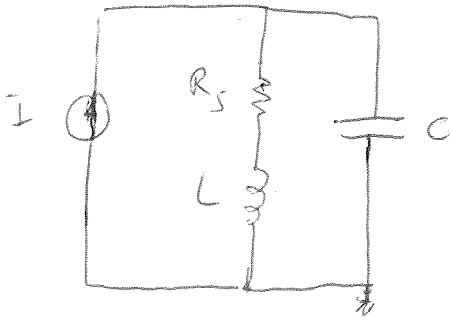

$$V = \frac{I}{j\omega C + \frac{1}{R_s + j\omega L}}$$

R_s przebiega wspaniałe, a ω $\rightarrow \omega_0$

$$\omega_0^2 = \frac{1}{LC}$$

$$j\omega C + \frac{1}{R_s + j\omega L} = 0 \quad \Delta RC + \Delta^2 LC + 1 = 0$$

$$\Delta^2 LC + \Delta RC + 1 = 0 \quad \Delta_{1,2} = -\frac{RC}{2LC} \pm \frac{1}{2LC} \sqrt{(RC)^2 - 4LC}$$

$$= -\frac{R}{2L} \pm j \frac{1}{LC} \sqrt{4C - \frac{(RC)^2}{4}} = -\frac{R}{2L} \pm j \frac{1}{LC} \sqrt{2C \left(1 - \frac{(RC)^2}{LC4}\right)} = \frac{1}{\omega_0^2}$$

$$= -\frac{R}{2L} \pm j \omega_0 \sqrt{1 - \frac{R^2 C}{4L}} = \left\{ C \frac{\omega_0^2}{L} \right\} = -\frac{R}{2L} \pm j \omega_0 \sqrt{1 - \frac{R^2 \omega_0^2}{4L}}$$

$$= -\frac{R}{2L} \pm j \omega_0 \sqrt{1 - \frac{(\omega_0 RC)^2}{4}}$$

$$C = \frac{1}{\omega_0^2 L}$$

$$Q = \frac{\omega_0 L}{R_s}$$

$$Q = \frac{1}{\omega_0 R_s C} = \frac{\omega_0 L}{R_s}$$


$$Q = \frac{1}{\omega_0 R_s C}$$

$$Q = \omega_0 R_p C$$

$$R_p = \frac{R_s}{Q^2}$$

$$Q = \omega_0 R_S Q^2 C = \frac{\omega_0 R_S C}{\omega_0^2 R_S^2 C^2} = \frac{1}{\omega_0 R_S C}$$

(5)

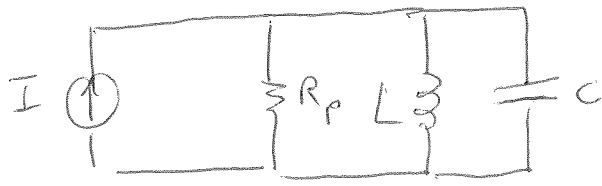

$$V = I R_p = I R_S Q^2$$


V molto elevata

Fattori di merito e qualità nei componenti

$$Q_{SL} = \frac{\omega_0 L}{R_S}$$


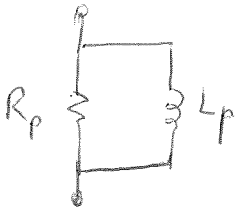
$$Z_{SL} = R_{SL} + j\omega L = j\omega L + \frac{\omega_0 L}{Q_{SL}}$$



$$Z = R_p \parallel j\omega L_p = \frac{R_p \cdot j\omega L_p (R_p - j\omega L_p)}{(R_p + j\omega L_p)(R_p - j\omega L_p)} =$$

$$= \frac{\omega^2 L_p^2 R_p + j\omega L_p R_p^2}{R_p^2 + \omega^2 L_p^2} = \frac{j\omega L_p R_p^2}{R_p^2 + \omega^2 L_p^2} + \frac{\omega^2 L_p^2 R_p}{R_p^2 + \omega^2 L_p^2} =$$

$$= \frac{j\omega L_p R_p^2}{R_p^2 \left(1 + \frac{\omega^2 L_p^2}{R_p^2}\right)} + \frac{\omega^2 L_p^2 R_p}{R_p^2 \left(1 + \frac{\omega^2 L_p^2}{R_p^2}\right)}$$

$$Q_{PL}^2 = \frac{R_p^2}{\omega^2 L_p^2}$$

$$= \frac{j\omega L_p}{1 + \frac{1}{Q^2}} + \frac{R_p}{Q_{PL}^2 \left(1 + \frac{1}{Q_{PL}^2}\right)}$$

(6)

$$Z_{SL} = Z_{PL}$$

$$L_p = L \left(1 + \frac{1}{Q_{PL}^2} \right) \approx L$$

$$R_p = R_{SL} Q_{PL}^2 \left(1 + \frac{1}{Q_{PL}^2} \right) \approx R_{SL} Q_{PL}^2$$

$$Q_{PL} = Q_{SL} = \frac{\omega L}{R_{SL}} = \frac{R_{pL}}{\omega L_p} = \frac{R_{pL}}{\omega L} = Q_L \quad \left\{ \begin{array}{l} Q_{pc} = \omega R_p C \\ Q_{sc} = \frac{1}{\omega R_s C} \end{array} \right.$$

CORR. dei FATTORI DI MERITO

$$Q_L = \frac{\omega L}{R_{SL}}$$


$$Q_c = \omega R_{pc} C$$

$$R_s = \frac{R_p}{1 + Q_{pc}^2}$$

$$C_s = C \left(1 + \frac{1}{Q_{pc}^2} \right)$$

$$Q_L = \frac{R_{pL}}{\omega L}$$

$$Q_c = \frac{1}{\omega R_s C}$$

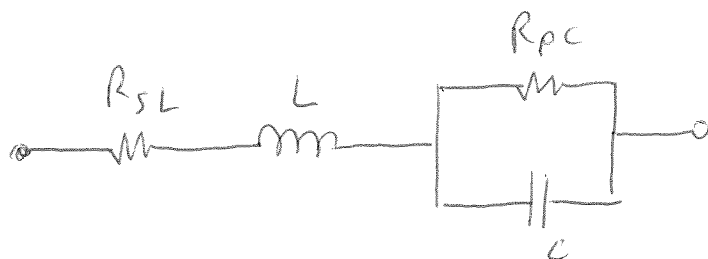

$$Z = R_{SL} + j\omega L + \frac{R_{pc}}{1 + j\omega R_{pc} C} = R_{SL} + j\omega L + \frac{R_{pc} (1 - j\omega R_{pc} C)}{(1 + j\omega R_{pc} C)(1 - j\omega R_{pc} C)} =$$

$$= R_{SL} + j\omega L + \frac{R_{pc}}{1 + \omega^2 R_{pc}^2 C^2} - \frac{j\omega R_{pc}^2 C}{1 + \omega^2 R_{pc}^2 C^2}$$

$$= \frac{\omega L}{Q_L} + \frac{R_{pc} \cdot \omega C}{\omega C (1 + \omega^2 R_{pc}^2 C^2)} + j\omega L - \frac{j\omega^2 R_{pc}^2 C^2}{\omega C (1 + \omega^2 R_{pc}^2 C^2)} =$$


$$= \underbrace{\frac{\omega L}{Q_L} + \frac{Q_c}{\omega C (1 + Q_c^2)}}_{R_{XSL}} + j\omega L - j \frac{Q_c^2}{\omega C (1 + \omega^2 R_p^2 C^2)}$$

$$\frac{\omega L}{Q} = \frac{\omega L}{Q_L} + \frac{Q_C}{\omega C(1+Q_C^2)}$$

$$\frac{1}{Q} = \frac{1}{Q_L} + \frac{Q_C}{1+Q_C^2} \approx \frac{1}{Q_L} + \frac{1}{Q_C}$$

—————

Reten de Colpitts

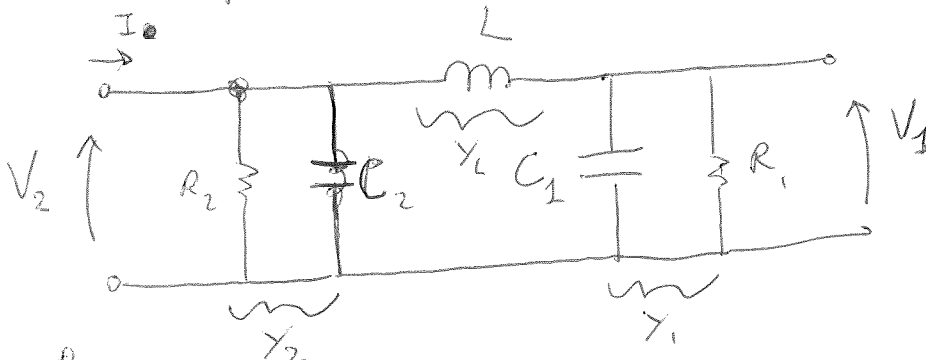

$$\begin{cases} V_2 Y_2 + (V_2 - V_1) Y_L = I \\ (V_2 - V_1) Y_L - V_1 Y_1 = 0 \end{cases}$$

$$V_1(s) = \frac{I}{s^3 L C_1 C_2 + s^2 (L C_1 G_2 + L C_2 G_1) + s (C_1 + C_2 + L G_1 G_2) + G_1 + G_2}$$

$$s^3 + s^2 \frac{C_1 G_2 + C_2 G_1}{L C_1 C_2} + s \frac{C_1 + C_2 + L G_1 G_2}{L C_1 C_2} + \frac{G_1 + G_2}{L C_1 C_2} = 0$$

$$a_3 s^3 + s^2 a_2 + s a_1 + a_0 = 0$$

$$s_0, s_1, s_2,$$

• fup. d. vobauke

(8)

$$-j\omega^3 + j\omega \frac{C_1 + C_2 + L G_1 G_2}{L C_1 C_2} = 0$$

$$\omega_0^2 = \frac{C_1 + C_2}{L C_1 C_2} + \frac{G_1 G_2}{C_1 C_2} = \frac{1}{L \frac{C_1 C_2}{C_1 + C_2}} + \frac{1}{R_1 C_1 R_2 C_2}$$

$$\alpha_0 = -\alpha_0 \alpha_1 \alpha_2 = \frac{G_1 + G_2}{L C_1 C_2} = -\delta_0 |\Delta_1|^2$$

$$\delta_0 = -\frac{G_1 + G_2}{L C_1 C_2} \cdot \frac{1}{\omega_0^2} \approx -\frac{G_1 + G_2}{L C_1 C_2 \cdot \frac{(C_1 + C_2)}{L C_1 C_2}} = -\frac{G_1 + G_2}{C_1 + C_2}$$

$$\alpha_2 = -(\alpha_1 + \alpha_2 + \alpha_0)$$

$$-(\alpha_1 + \alpha_2) = -2 \operatorname{Re}[\Delta_1] = 2\alpha = \alpha_0 + \alpha_2 =$$

$$2\alpha = -\frac{G_1 + G_2}{C_1 + C_2} + \cancel{\frac{C_1 G_2 + C_2 G_1}{L C_1 C_2}}$$

$$= \frac{-\cancel{C_1 C_2} (G_1 + G_2) + (C_1 + C_2) C_1 G_2 + (C_1 + C_2) (C_2 G_1)}{\cancel{C_1 C_2} (C_1 + C_2)} =$$

$$= -\frac{\cancel{C_1 C_2} G_1 - \cancel{C_1 C_2} G_2 + C_1^2 G_2 + C_1 C_2 G_2 + \cancel{C_1 C_2} G_1 + C_2^2 G_1}{C_1 C_2 (C_1 + C_2)}$$

$$2\alpha = \frac{C_1^2 G_2 + C_2^2 G_1}{C_1 C_2 (C_1 + C_2)} =$$

$$Q = \frac{\beta}{2\alpha} = \frac{\omega_0^2 C_1 C_2 (C_1 + C_2)}{C_1^2 G_2 + C_2^2 G_1} = \frac{\omega_0^2 C_1 C_2 (C_1 + C_2)}{\omega_0 C_1^2 \frac{1}{R_2} + \omega_0 C_2^2 \frac{1}{R_1}} =$$

$$= \frac{\omega_0^2 C_1 C_2 R_1 R_2 (C_1 + C_2)}{\omega_0 C_1 R_1 C_1 + \omega_0 C_2 R_2 C_2} = \frac{Q_{C_1} Q_{C_2} (C_1 + C_2)}{C_1 Q_{C_1} + C_2 Q_{C_2}}$$

$$C_1 \gg C_2$$

$$Q_1 \gg Q_2 \quad \approx \quad Q_{C_2} \left(1 + \frac{C_2}{C_1}\right) \approx Q_{C_2}$$

$$V_1(\omega_0) = \frac{I}{\omega_0^2 C_1 C_2} \frac{I}{-\omega_0^2 (L C_1 C_2 + L C_2 G_1) + G_1 + G_2}$$


$$= - \frac{I}{(C_1 + C_2) \left(\frac{G_2}{C_2} + \frac{G_1}{C_1} \right) + G_1 + G_2} = - \frac{I}{G_2 \frac{C_1}{C_2}}$$

$$V_1(\omega_0) = - I R_2 \left(\frac{C_2}{C_1} \right)$$

$$R_{in}(\omega_0) = R_1 \left(\frac{C_1}{C_2} \right)^2 \Rightarrow V_2 \approx I R_2$$

$$V_1 = - \frac{V_2}{R_2} R_2 \left(\frac{C_2}{C_1} \right) = - V_2 \frac{C_2}{C_1}$$

Hartley

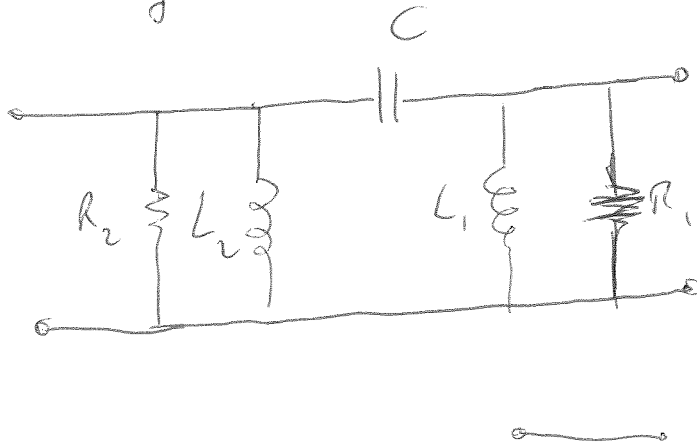

Coeff. of stability

$$S_F = \omega_0 \left| \frac{d\phi}{d\omega} \right|_{\omega=\omega_0}$$

Risuntando nwc



$$I = \frac{V}{R + j\omega L + \frac{1}{j\omega C}}$$

$$\phi = -\arctan \frac{b}{a} = \arctan \frac{\omega L - \frac{1}{\omega C}}{R} = -\arctan \frac{\omega L \left(1 - \frac{\omega_0^2}{\omega^2}\right)}{R}$$

$$\frac{d\phi}{d\omega} = - \frac{1}{1 + \left[\frac{\omega L \left(1 - \frac{\omega_0^2}{\omega^2}\right)}{R} \right]^2} \cdot \left[\frac{\omega L}{R} \left(1 - \frac{\omega_0^2}{\omega^2}\right) + \frac{\omega L}{R} \cdot \frac{\omega_0^2}{\omega^4} 2\omega \right] \Bigg|_{\omega=\omega_0}$$

$$= +\omega_0^2 \frac{\omega_0 L}{R} \frac{2\omega_0}{\omega_0^4} = \frac{2L\omega_0^2}{R\omega_0^2} = \frac{2L}{R}$$

$$S_F = \frac{\omega_0 2L}{R} = 2Q$$

$\uparrow$ $\uparrow$

(11)

$$SF = \omega_0 \left. \frac{d\varphi}{d\omega} \right|_{\omega=\omega_0}$$

$$V = \frac{I}{(1-s_0)(1-s_1)(1-s_2)}$$

$$V(j\omega) = \frac{I}{(j\omega - s_0)(j\omega - s_1)(j\omega - s_2)} = \frac{I}{(j\omega - s_0)(j\omega - \alpha - j\omega_0)(j\omega - \alpha + j\omega_0)}$$

$$SF = \omega_0 \left| \frac{d\varphi_0}{d\omega} + \frac{d\varphi_1}{d\omega} + \frac{d\varphi_2}{d\omega} \right|$$

$$\varphi_0 = \operatorname{arctg} \frac{\omega}{|s_0|}$$

$$\frac{d\varphi_0}{d\omega} = \frac{1}{1 + \frac{\omega_0^2}{|s_0|^2}} \cdot \frac{1}{s_0} = \frac{s_0}{\omega_0^2}$$

$$\varphi_1 = \operatorname{arctg} \frac{\omega_0 + \omega}{\alpha}$$

$$\frac{d\varphi_1}{d\omega} = \frac{1}{1 + \left(\frac{\omega_0 + \omega}{\alpha}\right)^2} \cdot \frac{1}{\alpha} = \frac{\alpha}{2\omega_0^2}$$

$$\varphi_2 = \operatorname{arctg} \frac{\omega_0 - \omega}{\alpha}$$

$$\frac{d\varphi_2}{d\omega} = \frac{1}{1 + \left(\frac{\omega_0 - \omega}{\alpha}\right)^2} \cdot \frac{1}{\alpha} = \frac{1}{\alpha}$$

$$SF = \omega_0 \cdot \frac{1}{\alpha} = \frac{\omega_0}{\alpha} = \frac{\beta}{\alpha} = 2 \text{ dB}$$

• Oscillation number 1 in assun di asinc

~~Conservazione dell'ENERGIA~~


• $A_f(s) = \frac{A(s)}{1 + A(s)f(s)}$

$1 + A(s)f(s) = 0$

1


$\Delta_{1,2} = \sigma_0 \pm j\omega_0$

$\sigma_0 > 0$

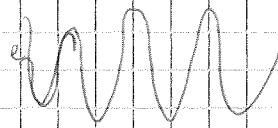


$\Downarrow$
 $2 e^{\sigma_0 t} \cos(\omega_0 t) \Rightarrow$

$\sigma_0 < 0$

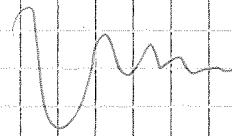

$\sigma_0 = 0$

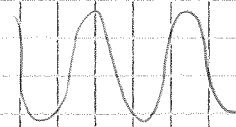

$s = j\omega$

$1 + f(j\omega)A(j\omega) = 0$

$\begin{cases} \text{Re} [1 + f(j\omega)A(j\omega)] = -1 \\ \text{Im} [1 + f(j\omega)A(j\omega)] = 0 \end{cases}$

fig. 2.1


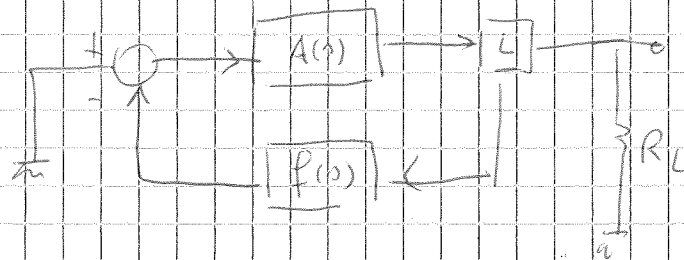





fig. 2.2

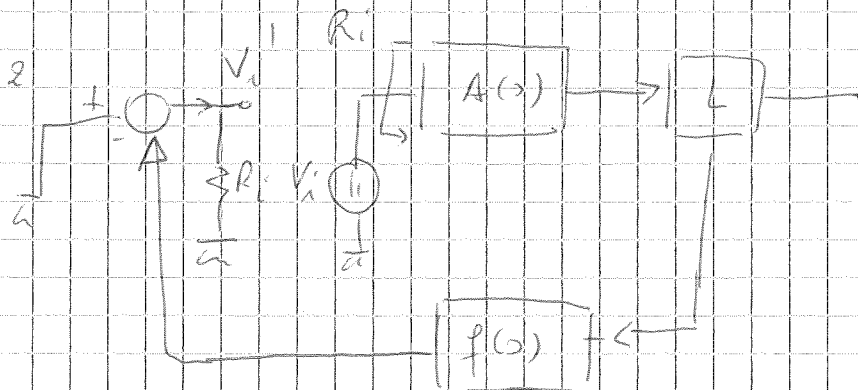


$V_L = V_i$

$-V_o A(s)f(s) = V_i \quad A(j\omega)f(j\omega) = -1$

Runners

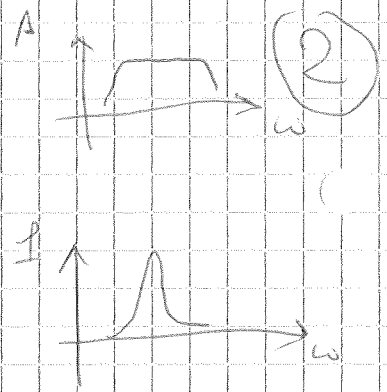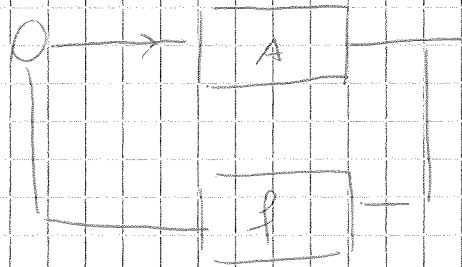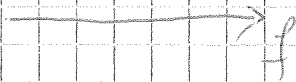

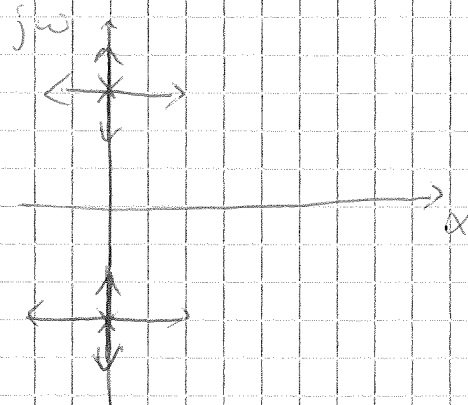Discours sulle condizioni MATERNITÀ di BARKHAUS



Variazione di amplitudine $\Rightarrow \Delta \omega > 0$

Variazione di fase

si osserva a ω_0 $\varphi(\omega_0) = \pi$

$\varphi(\omega_0) \neq \pi$

$$\varphi(\omega) = \varphi(\omega_0) + \left. \frac{d\varphi}{d\omega} \right|_{\omega=\omega_0} (\omega - \omega_0)$$

$$\omega_0' \quad \varphi(\omega_0') = \pi$$

$$\pi = \varphi(\omega_0) + \left. \frac{d\varphi}{d\omega} \right|_{\omega=\omega_0} (\omega_0' - \omega_0)$$

$$\Delta\varphi = \pi - \varphi(\omega_0) \quad \Delta\omega = \omega_0' - \omega_0$$


$$\Delta\varphi = \left. \frac{d\varphi}{d\omega} \right|_{\omega=\omega_0} \Delta\omega$$

$$S_F = \omega_0 \left. \frac{d\varphi}{d\omega} \right|_{\omega=\omega_0} \Rightarrow \Delta\omega = \frac{\Delta\varphi}{S_F} \omega_0$$

$S_F \Rightarrow \omega$

Oscillator di Wien

3

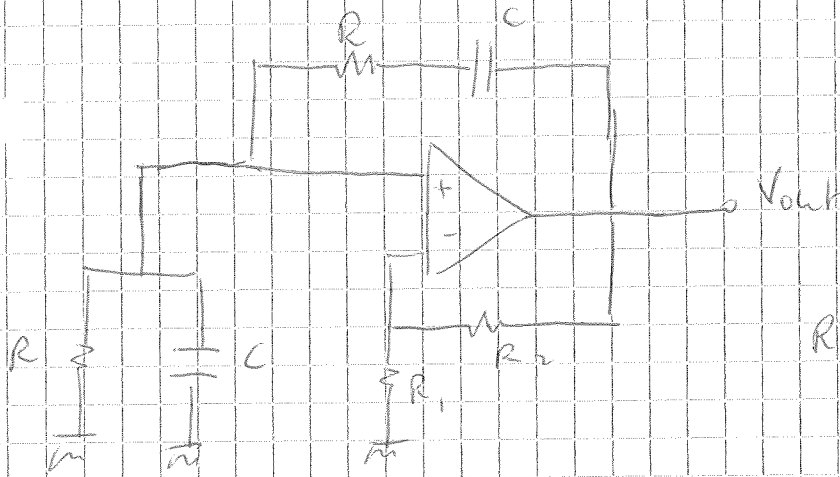

$$R // \frac{1}{sC} = \frac{R}{1+sRC}$$

$$V^+ = V_{out} \cdot \frac{R // \frac{1}{sC}}{R // \frac{1}{sC} + R + \frac{1}{sC}} = \frac{\frac{R}{1+sRC}}{\frac{R}{1+sRC} + R + \frac{1}{sC}} = \frac{\frac{R}{1+sRC}}{\frac{R + sRC(1+sRC)R + 1 + sRC}{(1+sRC)sC}} = \frac{sRC}{s^2R^2C^2 + 3sRC + 1} \Rightarrow$$

$$\Rightarrow \frac{V^+}{V_{out}} = f = \frac{sRC}{s^2R^2C^2 + 3sRC + 1}$$

$$A = 1 + \frac{R_2}{R_1}$$

$$\left(1 + \frac{R_2}{R_1}\right) \left(\frac{sRC}{s^2R^2C^2 + 3sRC + 1}\right) = f_A = 1$$

$$f(j\omega) = \frac{j\omega RC}{-\omega^2 R^2 C^2 + 3j\omega RC + 1}$$

$$\text{Im}[f(j\omega)A(j\omega)] = 0$$


$$\omega_0^2 = \frac{1}{R^2 C^2}$$

$$\omega_0 = \frac{1}{RC}$$

$$f(j\omega_0) = \frac{j\omega_0 RC}{3j\omega_0 RC} = \frac{1}{3}$$

$$\left(1 + \frac{R_2}{R_1}\right) \cdot \frac{1}{3} \geq 1$$

$$1 + \frac{R_2}{R_1} = 3 + \epsilon$$

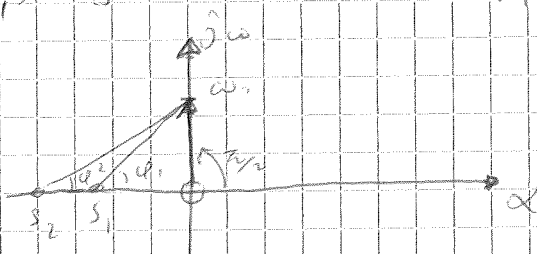

$$\Delta_{1,2} = -\frac{3}{2RC} \pm \frac{1}{2RC} \sqrt{9R^2C^2 - 4R^2C^2}$$

$$= -\frac{3}{2RC} \pm \frac{\sqrt{5}}{2RC}$$

$$S_F = \omega_0 \left. \frac{d\varphi}{d\omega} \right|_{\omega=\omega_0}$$

(4)



$$f(j\omega) = \frac{j\omega RC}{-\omega^2 R^2 C^2 + 3j\omega RC + 1} = \frac{1}{3j\omega RC + 3 - \frac{1}{\omega RC}}$$

$$\varphi = \angle f(j\omega) = \arctan \frac{\omega RC - \frac{1}{\omega RC}}{3}$$

$$\frac{d\varphi}{d\omega} = \frac{1}{1 + \underbrace{\left(\omega RC - \frac{1}{\omega RC} \right)^2}_9} \cdot \frac{RC + \frac{1}{\omega^2 RC}}{3} \bigg|_{\omega=\omega_0} = \frac{2RC}{3}$$

$$S_F = \omega_0 \frac{2RC}{3} = \frac{2}{3}$$

Operation des Oszillators

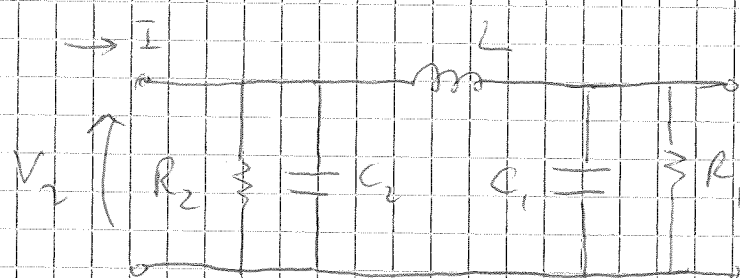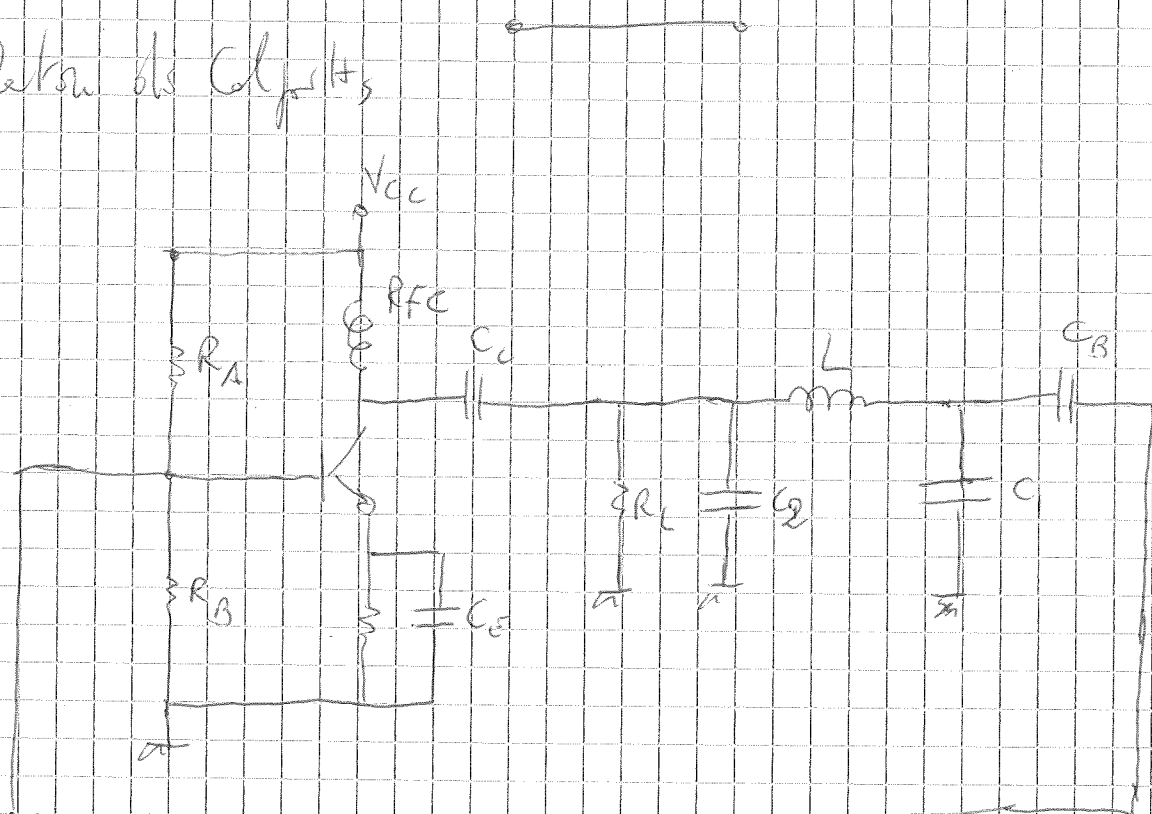

$$V_1 = -R_2 I \frac{C_2}{C_1}$$

$$R_{in} = R \frac{C_1}{C_2}$$

$$C_1 \gg C_2$$

$$R_2 = R_L$$

$$R_1 = R_A // R_B // R_{\pi}$$

$$\omega_0 = \frac{1}{\sqrt{L(C_1 C_2)}}$$

(4)

$$I = -g_m \tilde{v}_{BE}$$

$$v_1 = +g_m \tilde{v}_{BE} \cdot R_L \frac{C_2}{C_1} = v_{BE}$$

$$g_m R_L \frac{C_2}{C_1} = 1$$

$$g_m = \frac{C_1}{C_2} \frac{1}{R_L}$$

$$I_C = \frac{C_1}{C_2} \frac{V_T}{R_L}$$