

## Practical Session 2

### Transformers and Mixers

#### Aim

To investigate the behaviour and frequency response of RF transformers and Double Balanced Mixers and to reinforce the theory of transformers and mixers, described in Chapter 3 “RF Transformers” and Chapter 5 “Mixers” of the RF Electronics Lecture notes by C. J. Kikkert and distributed through AWR Corp.

#### Procedure

- 1 For the transformer core given, calculate the Leakage and Magnetising Inductance of a trail winding on the transformer. Hence make two transformer cores suitable for use in a double balanced mixer, to have a  $50 \Omega$  impedance at 1 MHz.
- 2 Measure the frequency response of the transformer, when connected as 1:1 turns ratio isolation transformer.
- 3 Match 4 Shottky Barrier Diodes and construct the double balanced mixer. Measure the useful frequency range of the mixer and at the low, mid and high frequency range:
  - Measure the local oscillator isolation.
  - Measure the unwanted frequency components.
  - Measure the conversion loss.
  - Plot the spectrum for the mixer used as a Double Sideband Modulator.
  - Investigate the spectra of the mixer at the harmonics of the local oscillator.

#### Equipment required

RF Transformer cores, like Neosid 28-512-31 cores 12.7mm dia x 6.4mm high torroid with F14 ferrite and a 6.4 mm dia hole. 2 cores per mixer.

4 matched shottky-barrier diodes, PCB with BNC connectors for mounting mixer. See Fig 34 of Chapter 5 “Mixers” for suitable example. Double sided PCB with 3 BNC connectors soldered to it can also be used.

RF Signal Generator (up to 100 MHz)  $>+7\text{dBm}$  output, Spectrum Analyser, Cathode Ray Oscilloscope, Low frequency (100Hz-1MHz) Sinewave generator ( $50 \Omega$  output).

Further details: please email [Keith.Kikkert@jcu.edu.au](mailto:Keith.Kikkert@jcu.edu.au).