

**RADIOFREQUENCY ELECTRONIC SYSTEMS 2018-2019**

<b>1</b>	<b>AMOROSO</b>	<b>FEDERICO</b>	<b>amoroso.1709028@studenti.uniroma1.it</b>
	<b>LIOTTA</b>	<b>MATTEO</b>	<b>matteoliotta12@gmail.com</b>
	<b>PALOMBI</b>	<b>ALESSANDRO</b>	<b>palombi.1646957@studenti.uniroma1.it</b>
	<b>PAPARELLO</b>	<b>DANIELE</b>	<b>paparello.1702326@studenti.uniroma1.it</b>
	<p><b>Colpitts Oscillator, load = 1 k<math>\Omega</math>, VCC=10 V</b>  <b>Transistor BFP520, 1 MHz</b></p> <p><b><a href="http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/">http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/</a></b></p>		
<b>2</b>	<b>ANTUONO</b>	<b>CHIARA</b>	<b>chiaraantuono18@gmail.com</b>
	<b>IMPERATO</b>	<b>FRANCESCA</b>	<b>francescaimpe@gmail.com</b>
	<b>RICCI</b>	<b>GIANMARCO</b>	<b>gianmarco-ricci@live.it</b>
	<p><b>Ceramic Oscillator Vcc = 2 V, 50<math>\Omega</math></b>  <b>Transistor NE3508M4 2450 MHz</b></p> <p><b><a href="http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/">http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/</a></b></p>		

<b>3</b>	<b>BENSHABAN</b>	<b>ROUA</b>	<b>benshaban.1841719@studenti.uniroma1.it</b>
	<b>BRONZI</b>	<b>DARIO</b>	<b>dariovaleriobronzi@libero.it</b>
	<b>LUCIARINI</b>	<b>MANUEL</b>	<b>luciarini.1706270@studenti.uniroma1.it</b>
	<b>PANICO</b>	<b>AMEDEO</b>	<b>ame93@live.it</b>
	<p><b>Low Pass filter with lumped elements and STEP microstrip lines</b>  <math>F_t = 4000 \text{ MHz}</math> 3 dB  Out of band: 4800 MHz 10 dB  Binomial response</p>		
<b>4</b>	<b>CALDANI</b>	<b>FILIPPO</b>	<b>filippo.caldani@gmail.com</b>
	<b>DELLA MORTE</b>	<b>RODRIGO</b>	<b>2rodrigodm@gmail.com</b>
	<b>LIMA</b>	<b>ERIKA</b>	<b>lima.1638254@studenti.uniroma1.it</b>
	<p><b>Ceramic Oscillator <math>V_{cc} = 2 \text{ V}</math>, <math>50\Omega</math></b>  Transistor NE3508M4 900 MHz   <a href="http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/">http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/</a></p>		

<b>5</b>	<b>CAMPONESCHI</b>	<b>FEDERICO</b>	<b>camponeschi.1706052@studenti.uniroma1.it</b>
	<b>DI GIORGIO</b>	<b>ALESSIO</b>	<b>digiorgio.1653629@studenti.uniroma1.it</b>
	<b>JANNI</b>	<b>FEDERICO</b>	<b>janni.1603864@studenti.uniroma1.it</b>
	<p><b>Gain Amplifier with Unconditionally stable Transistor + Layout</b>  Transistor BFU530X, 5V – 20 mA, f = 3 GHz</p> <p><b><a href="http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/">http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/</a></b></p>		
<b>6</b>	<b>CARLOMAGNO</b>	<b>ANTONIO</b>	<b>carlomagno.1693552@studenti.uniroma1.it</b>
	<b>PANTIRU</b>	<b>CLAUDIO</b>	<b>pantiru.1705328@studenti.uniroma1.it</b>
	<b>AMBROGIONI</b>	<b>VERONICA</b>	
	<p><b>Class A Power Amplifier f = 2 GHz</b>  Transistor GaN GP1441 48V-200 mA Pin 0.5 W</p> <p><b><a href="http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/">http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/</a></b></p>		

<b>7</b>	<b>CHOLLANGI</b>	<b>VENKATA KISHORE</b>	<b>venkatakishorechollangi@gmail.com</b>
	<b>JAGABATHUNI</b>	<b>SATYA SAI</b>	<b>satyasai.ss81@gmail.com</b>
	<b>KOTTA</b>	<b>MANIDEEP</b>	<b>koma27011994@gmail.com</b>
	<b>MERUGA</b>	<b>PHANIDEEP</b>	<b>merugaphani7@gmail.com</b>
	<p><b>Low Pass filter with lumped elements and STEP microstrip lines</b>  <math>F_t = 5000</math> MHz 3 dB  Out of band: 6000 MHz 30 dB  Constant ripple response</p>		
<b>8</b>	<b>CORNAGGIA</b>	<b>FLAVIO</b>	<b>flavio.cornaggia@gmail.com</b>
	<b>GIRALDI</b>	<b>LORENZO</b>	<b>giraldi.1649909@studenti.uniroma1.it</b>
	<b>OLIVIERI</b>	<b>ENNIO</b>	<b>olivieri.1668323@studenti.uniroma1.it</b>
	<p><b>Low Pass filter with lumped elements and COMMENSURATE microstrip lines</b>  <math>F_t = 2000</math> MHz 3 dB  Out of band: 3000 MHz 10 dB  Binomial response</p>		

<b>9</b>	<b>DELLA SALA</b>	<b>RICCARDO</b>	<b>riccardo.della.sala@gmail.com</b>
	<b>INGO</b>	<b>PIERFRANCESCO MARIA</b>	<b>pier.ingo@gmail.com</b>
	<b>SABBADINI</b>	<b>MATTEO</b>	<b>matteosabbadini96@libero.it</b>
<p><b>Class A Power Amplifier <math>f = 1</math> GHz</b>  Transistor GaN GP1441 24V-400 mA, Pin 0.5 W</p> <p><b><a href="http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/">http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/</a></b></p>			
<b>10</b>	<b>GHA SEMI</b>	<b>MARYAM</b>	<b>maryam.qasemi12@gmail.com</b>
	<b>JAVAHERI</b>	<b>PEYMAN</b>	<b>javaheri.1872189@studenti.uniroma1.it</b>
	<b>KIANBAKHT</b>	<b>NASTARAN</b>	<b>kianbakht.1873606@studenti.uniroma1.it</b>
	<b>RASTKHIZ</b>	<b>ALI</b>	<b>rastkhizlalehmarzi.1782488@studenti.uniroma1.it</b>
<p><b>Low Noise Amplifier, <math>M_{Lout} = 1</math></b>  Transistor BFU530X, 5V – 20 mA, <math>f = 3</math> GHz</p> <p><b><a href="http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/">http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/</a></b></p>			

<b>11</b>	<b>ERCOLANI</b>	<b>ANDREA</b>	<b>ercolani.1634621@studenti.uniroma1.it</b>
	<b>MASSAIOLI</b>	<b>SERGIO</b>	<b>massaioli.1692695@studenti.uniroma1.it</b>
	<p><b>Colpitts Oscillator, load = 1 k<math>\Omega</math>, VCC=8 V</b>  Transistor BFP520, 5 MHz</p> <p><b><a href="http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/">http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/</a></b></p>		
<b>12</b>	<b>SAVAIA</b>	<b>ALESSIO</b>	<b>savaia.1642419@studenti.uniroma1.it</b>
	<b>TINTI</b>	<b>ALESSANDRO</b>	<b>aletinti96@gmail.com</b>
	<b>DI CIACCIO</b>	<b>VALERIO</b>	<b>valeriodiciaccio@hotmail.it</b>
	<p><b>Colpitts Oscillator, load = 1 k<math>\Omega</math>, VCC=6 V</b>  Transistor BFP520, 10 MHz</p> <p><b><a href="http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/">http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/</a></b></p>		

<b>13</b>	<b>D'ALBA</b>	<b>ALESSANDRO</b>	<b>alessandrodalba95@gmail.com</b>
	<b>DURANTE</b>	<b>SALVATORE</b>	<b>salvatore.durante11@gmail.com</b>
	<b>LOVICU</b>	<b>GABRIELE</b>	<b>lovicu.1867427@studenti.uniroma1.it</b>
	<p><b>Low Pass filter with lumped elements and COMMENSURATE microstrip lines</b>  <math>F_t = 3000</math> MHz 3 dB  Out of band: 3600 MHz 10 dB  Constant ripple response</p>		
<b>14</b>	<b>TASKAYA</b>	<b>AYCAN</b>	<b>taskaya.1873897@studenti.uniroma1.it</b>
	<b>EMMANUEL</b>	<b>NENWOLA</b>	<b>nemman_august@yahoo.fr</b>
	<b>VALIYEV</b>	<b>RAMAL</b>	<b>ramalvaliyev@gmail.com</b>
	<b>RASOAMAHENINA</b>	<b>PHILIPPE</b>	<b>Philippe.rasoamahenina@gmail.com</b>
	<p><b>Low Pass filter with lumped elements and COMMENSURATE microstrip lines</b>  <math>F_t = 1000</math> MHz 3 dB  Out of band: 1500 MHz 10 dB  Binomial response</p>		

<b>15</b>	<b>MARCHI</b>	<b>MARIANGELA</b>	<b>mariangela.marchi1993@gmail.com</b>
	<b>VAGNI</b>	<b>LORENZO</b>	<b>vagni.lorenzo@tiscali.it</b>
<p><b>Colpitts Oscillator, load = 1 k<math>\Omega</math> VCC=3 V</b>  <b>Transistor BFP520, 20 MHz</b></p> <p><b><a href="http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/">http://mwl.diet.uniroma1.it/people/pisa/RFELSYS/MATERIALE%20INTEGRATIVO/</a></b></p>			
	<b>PRIMOMO</b>	<b>LUCA</b>	<b>primomo.1351832@studenti.uniroma1.it</b>
	<b>ROMANELLO</b>	<b>ANDREA</b>	<b>andrearomanello93@gmail.com</b>