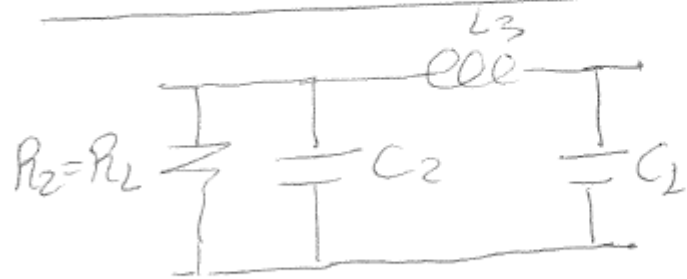


Progetto di base con MWO di un oscillatore Colpitts

Oscillatore $f = 1 \text{ MHz}$

carico $R_L = 1 \text{ k}\Omega$

$V_p \approx 10 \text{ V}$



$$Q = Q_2 = \omega_0 C_2 R_2 > 10$$

$$2\pi \cdot 10^6 \cdot C_2 \cdot 10^3 > 10$$

$$C_2 > \frac{10}{2\pi \cdot 10^9} \approx 1.6 \text{ nF}$$

$$\boxed{C_2 = 2.2 \text{ nF}}$$


$$C_2 \gg C_2 \approx 20 C_2 \Rightarrow \boxed{C_2 = 47 \text{ nF}}$$


$$\omega_0^2 = \frac{1}{L \frac{C_1 C_2}{C_1 + C_2}} \approx \frac{1}{L C_2}$$

$$f_0^2 (2\pi)^2 = \frac{1}{L C_2}$$


$$L = \frac{1}{f_0^2 (2\pi)^2 C_2} = \frac{1}{10^{12} \frac{36}{22} \times 10^{-9}} \approx 12 \mu\text{H}$$

negliamo $L = 10 \mu\text{H}$

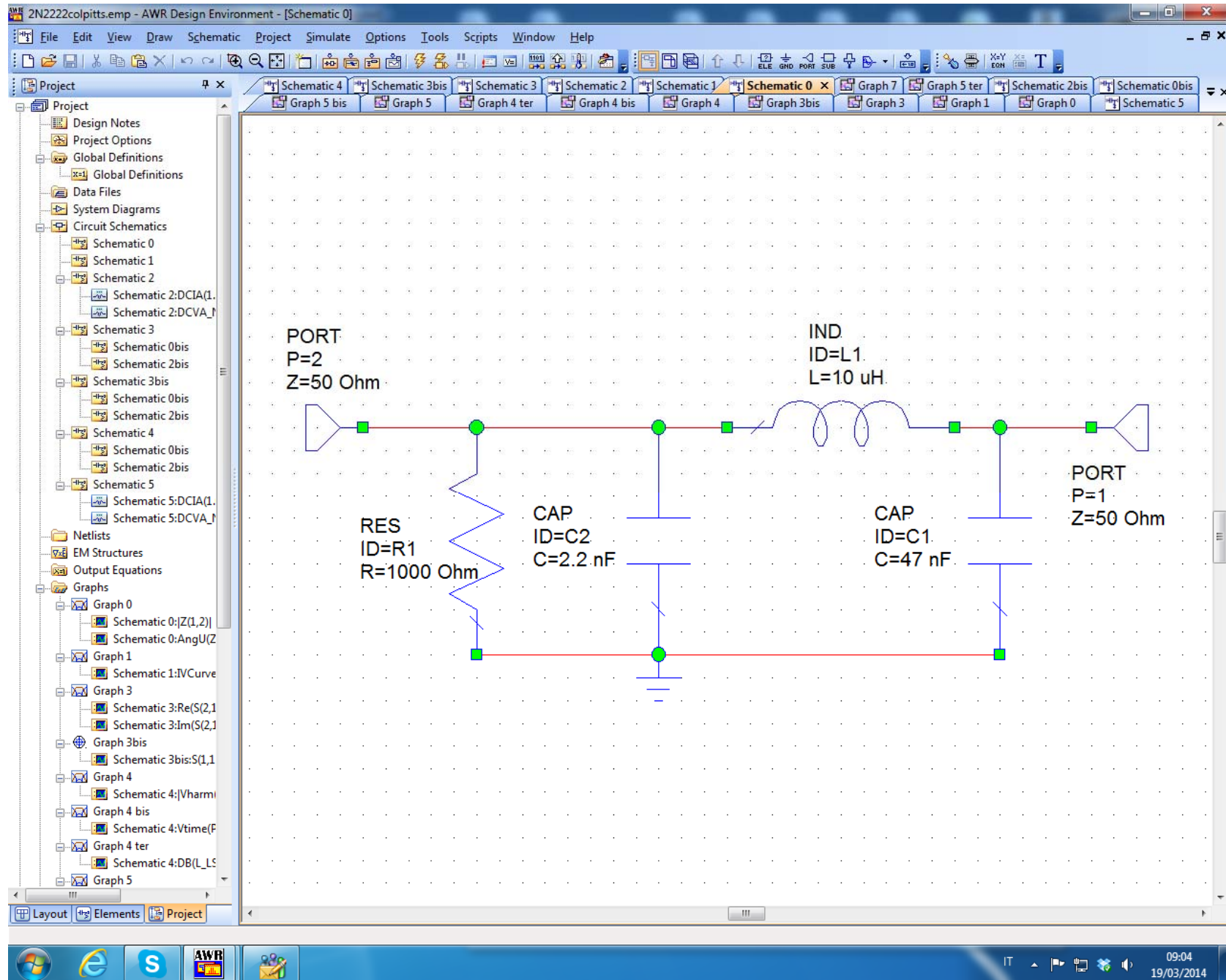

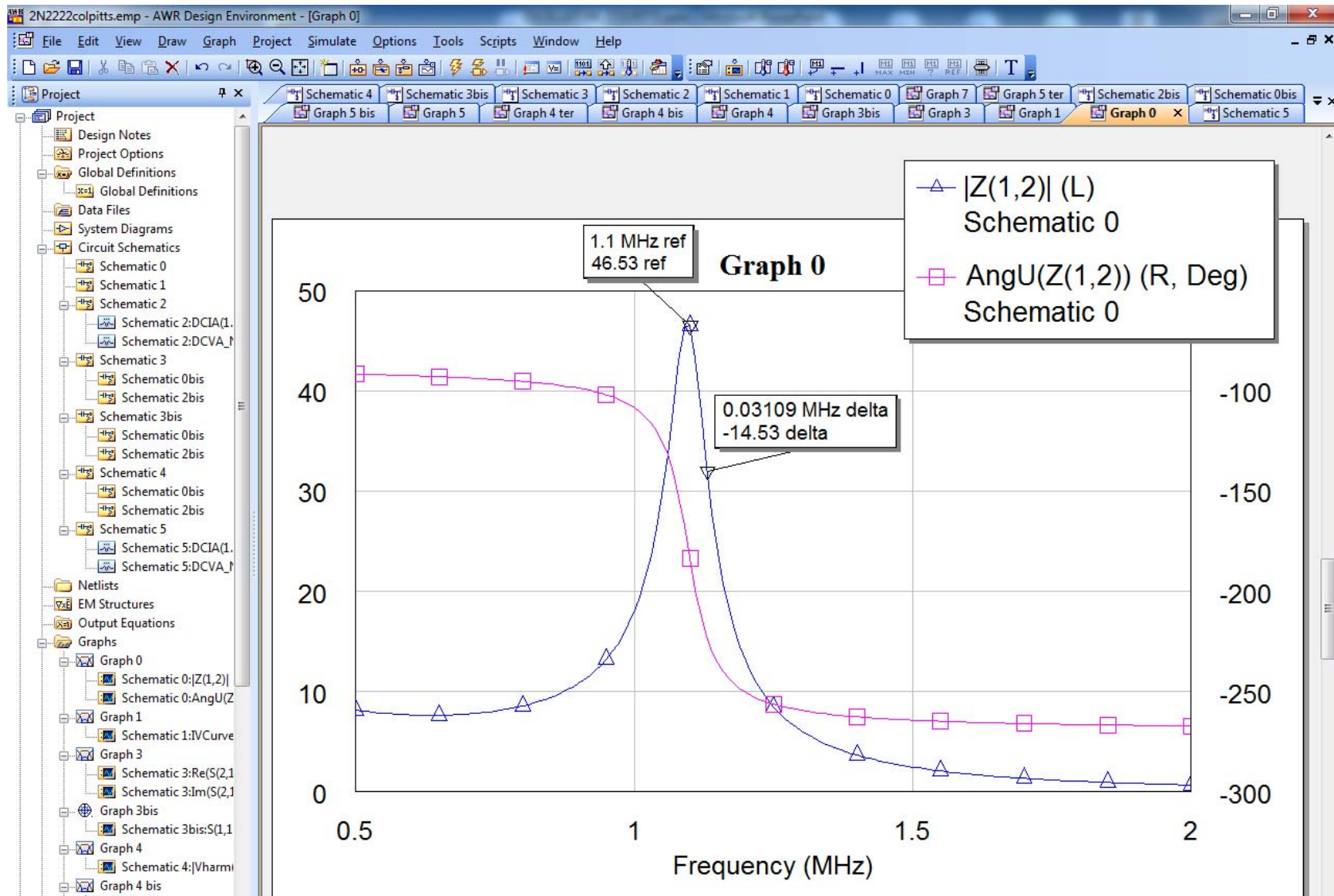

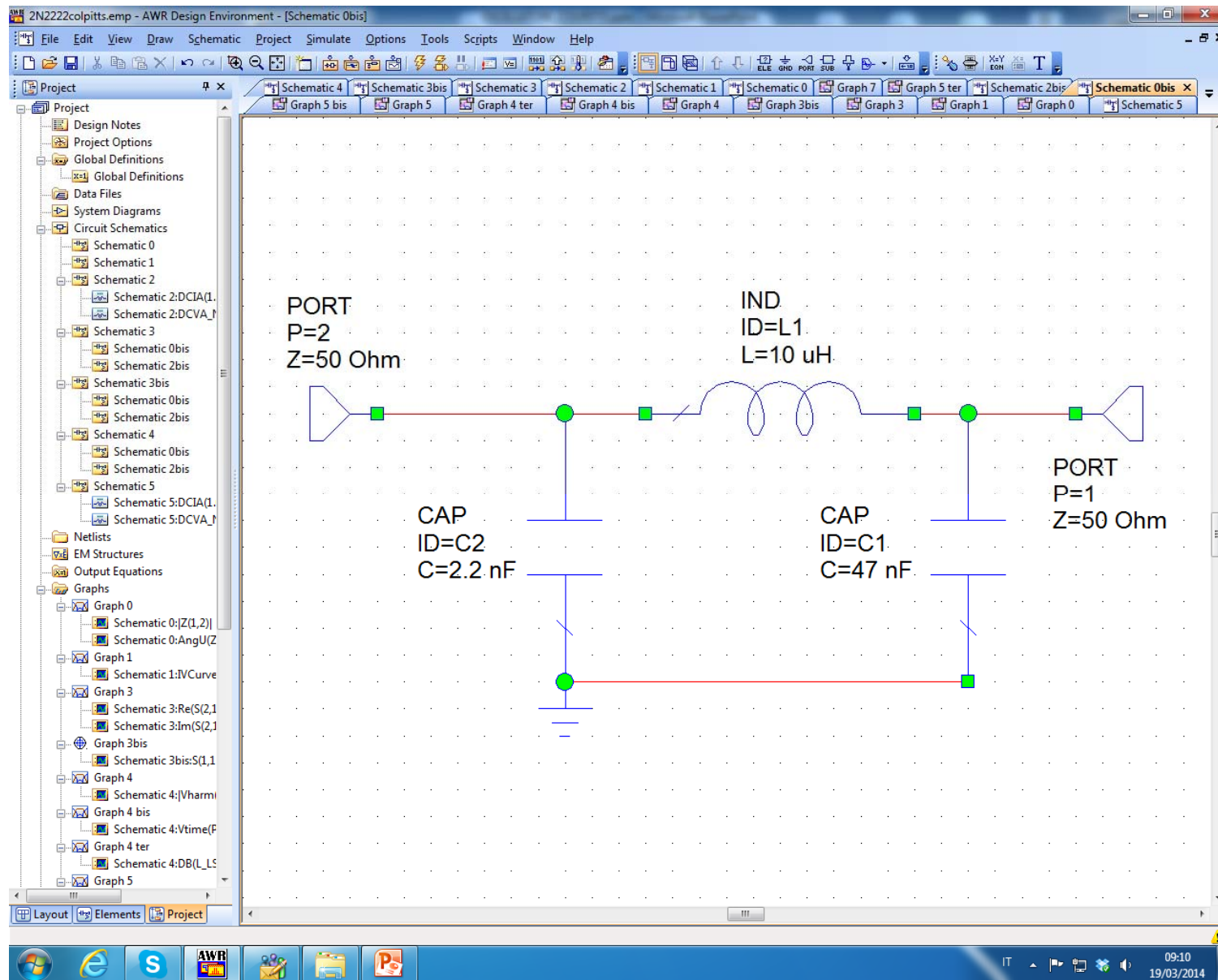Il fattore di merito del circuito vale $Q = 1.1/0.06 \cong 18$



Circuito bis senza il carico

2N2222colpitts.emp - AWR Design Environment - [Schematic 1]

File Edit View Draw Schematic Project Simulate Options Tools Scripts Window Help

Project

- Design Notes
- Project Options
- Global Definitions
 - Global Definitions
 - Data Files
- System Diagrams
- Circuit Schematics
 - Schematic 0
 - Schematic 1
 - Schematic 2
 - Schematic 2:DCIA(1)
 - Schematic 2:DCVA_1
 - Schematic 3
 - Schematic 0bis
 - Schematic 2bis
 - Schematic 3bis
 - Schematic 0bis
 - Schematic 2bis
 - Schematic 4
 - Schematic 0bis
 - Schematic 2bis
 - Schematic 5
 - Schematic 5:DCIA(1)
 - Schematic 5:DCVA_1
- Netlists
- EM Structures
- Output Equations
- Graphs
 - Graph 0
 - Schematic 0:|Z(1,2)|
 - Schematic 0:AngU(Z)
 - Graph 1
 - Schematic 1:IVCurve
 - Graph 3
 - Schematic 3:Re(S(2,1)
 - Schematic 3:Im(S(2,1)
 - Graph 3bis
 - Schematic 3bis:S(1,1)
 - Graph 4
 - Schematic 4:|Vharm|
 - Graph 4 bis
 - Schematic 4:Vtime(F)
 - Graph 4 ter
 - Schematic 4:DB(L_LS)
 - Graph 5

Schematic 4 Schematic 3bis Schematic 3 Schematic 2 Schematic 1 x Schematic 0 Graph 7 Graph 5 ter Schematic 2bis Schematic 0bis Graph 5 bis Graph 5 Graph 4 ter Graph 4 bis Graph 4 Graph 3bis Graph 3 Graph 1 Graph 0 Schematic 5


IVCURVE1
ID=IV1
VSWEEP_start=0 V
VSWEEP_stop=20 V
VSWEEP_step=0.1 V
ISTEP_start=0 mA
ISTEP_stop=0.1 mA
ISTEP_step=0.02 mA

GBJT
ID=GP_2n2222a_1

2 C
1 B
4 S
3 E

Swp Step

AWR 09:08 19/03/2014

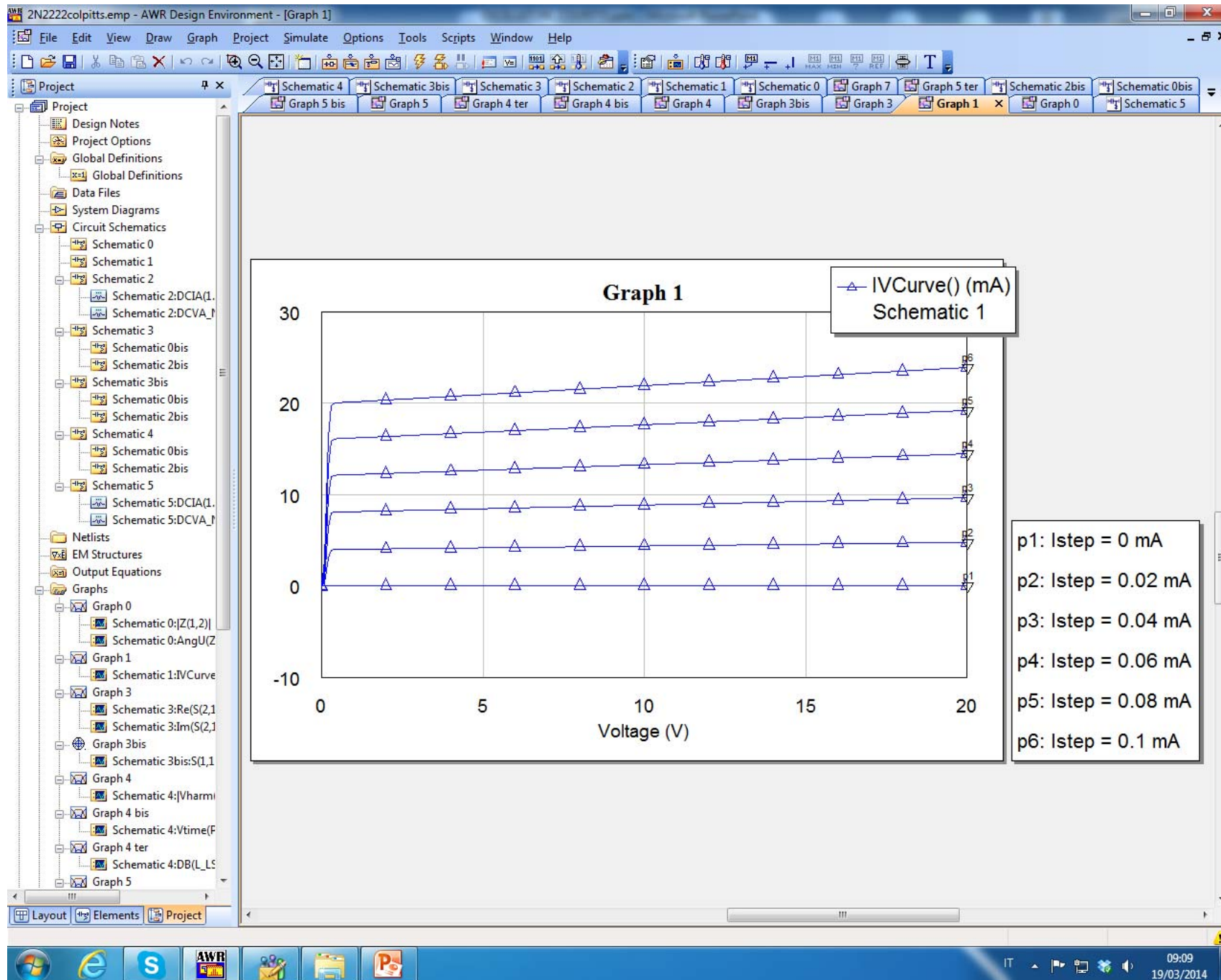


$$g_m R_2 \approx \frac{C_1}{C_2}$$

$$g_m = \frac{I_C}{V_T}$$

$$I_C \approx \frac{C_1}{C_2} \cdot \frac{V_T}{R_2} = \frac{47}{22} \cdot \frac{26 \times 10^{-3}}{10^3} = 0.56 \text{ mA}$$

$$I_C = 1 \text{ mA}$$

$$V_{CC} = 10 \text{ V}$$

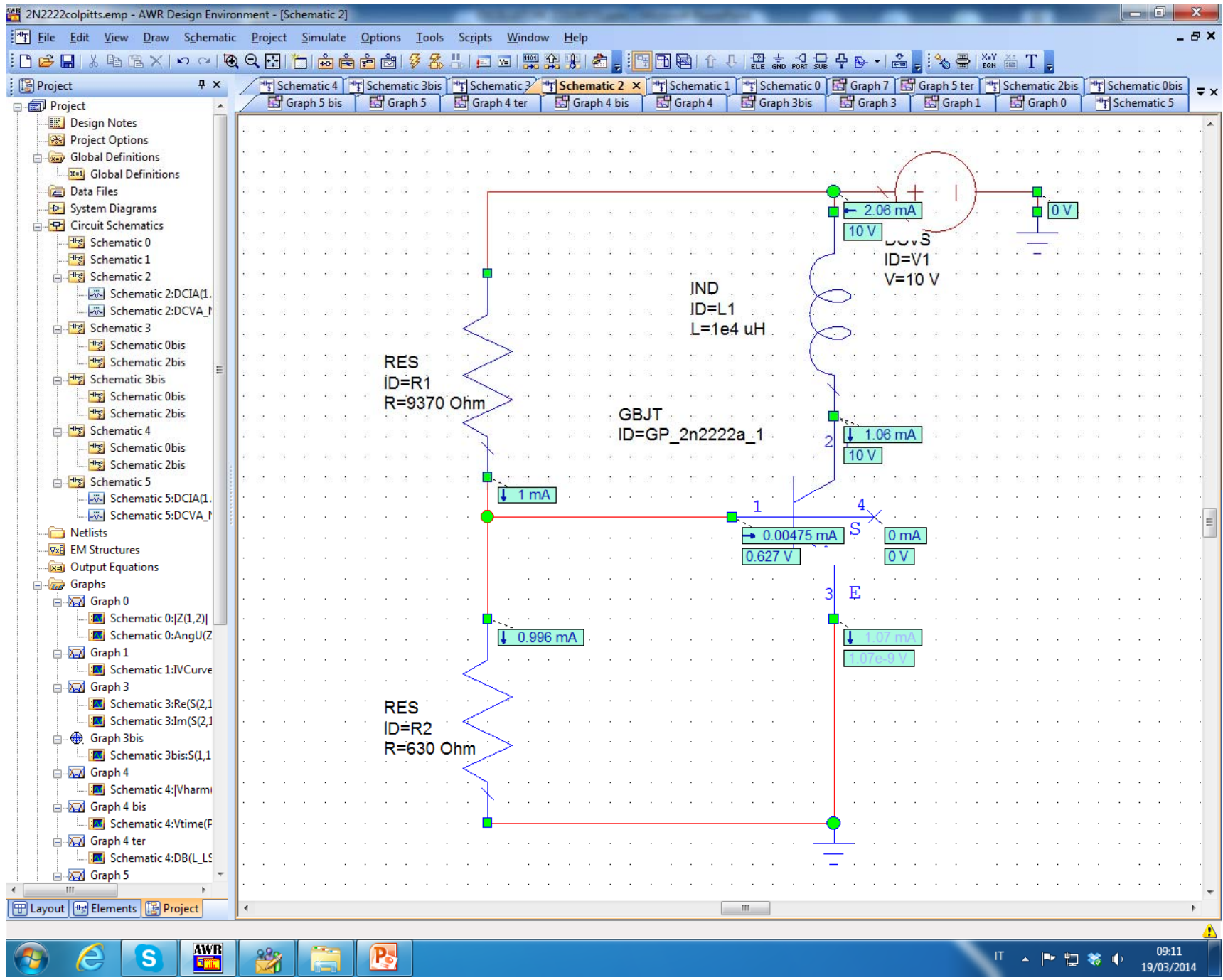

- La coppia di resistenze sulla base si determina a partire da una V_{be} di circa 0.6 V e poi per tentativi si cerca il valore che realizza $I_c = 1 \text{ mA}$
- (DRAW Add Annotation DCIA e DCVA_N
- L'induttanza L si dimensiona imponendo che la sua reattanza alla frequenza di oscillazione sia almeno 50 volte più grande della resistenza del carico
- I condensatori di blocco si dimensionano imponendo che la loro reattanza alla frequenza di oscillazione sia inferiore ad 1Ω

2N2222colpitts.emp - AWR Design Environment - [Schematic 2bis]

File Edit View Draw Schematic Project Simulate Options Tools Scripts Window Help

Project

- Design Notes
- Project Options
- Global Definitions
 - Global Definitions
- Data Files
- System Diagrams
- Circuit Schematics
 - Schematic 0
 - Schematic 1
 - Schematic 2
 - Schematic 2:DCIA(1)
 - Schematic 2:DCVA_1
 - Schematic 3
 - Schematic 0bis
 - Schematic 2bis
 - Schematic 3bis
 - Schematic 0bis
 - Schematic 2bis
 - Schematic 4
 - Schematic 0bis
 - Schematic 2bis
 - Schematic 5
 - Schematic 5:DCIA(1)
 - Schematic 5:DCVA_1
- Netlists
- EM Structures
- Output Equations
- Graphs
 - Graph 0
 - Schematic 0:|Z(1,2)|
 - Schematic 0:AngU(Z)
 - Graph 1
 - Schematic 1:IVCurve
 - Graph 3
 - Schematic 3:Re(S(2,1))
 - Schematic 3:Im(S(2,1))
 - Graph 3bis
 - Schematic 3bis:S(1,1)
 - Graph 4
 - Schematic 4:|Vharm|
 - Graph 4 bis
 - Schematic 4:Vtime(F)
 - Graph 4 ter
 - Schematic 4:DB(L_LS)
 - Graph 5

Layout Elements Project

DCVS
ID=V1
V=10 V

IND.
ID=L1
L=1e4 uH

CAP
ID=C1
C=1000 nF

GBJT
ID=GP_2n2222a_1

RES
ID=R1
R=9370 Ohm

RES
ID=R2
R=630 Ohm

PORT
P=1
Z=50 Ohm

PORT
P=2
Z=50 Ohm

1 B

2 C

3 E

4 S

09:11
19/03/2014

2N2222colpitts.emp - AWR Design Environment - [Schematic 3]

File Edit View Draw Schematic Project Simulate Options Tools Scripts Window Help

Project

- Design Notes
- Project Options
- Global Definitions
 - Global Definitions
- Data Files
- System Diagrams
- Circuit Schematics
 - Schematic 0
 - Schematic 1
 - Schematic 2
 - Schematic 2:DCIA(L)
 - Schematic 2:DCVA_I
 - Schematic 3
 - Schematic 0bis
 - Schematic 2bis
 - Schematic 3bis
 - Schematic 0bis
 - Schematic 2bis
 - Schematic 4
 - Schematic 0bis
 - Schematic 2bis
 - Schematic 5
 - Schematic 5:DCIA(L)
 - Schematic 5:DCVA_I
 - Netlists
 - EM Structures
 - Output Equations
 - Graphs
 - Graph 0
 - Schematic 0:|Z(1,2)|
 - Schematic 0:AngU(Z)
 - Graph 1
 - Graph 3
 - Schematic 1:IVCurve
 - Graph 3bis
 - Schematic 3:Re(S(2,1))
 - Schematic 3:Im(S(2,1))
 - Graph 4
 - Schematic 4:|Vharm|
 - Schematic 4:Vtime(F)
 - Schematic 4:DB(L_LS)
 - Graph 5

Schematic 3

OSCTEST ID=O1

SUBCKT ID=S2
NET="Schematic 2bis"

PORT P=1
Z=50 Ohm


PORT P=2
Z=50 Ohm


SUBCKT ID=S1
NET="Schematic 0bis"


PORT P=3
Z=1000 Ohm

Layout Elements Project

09:12
19/03/2014

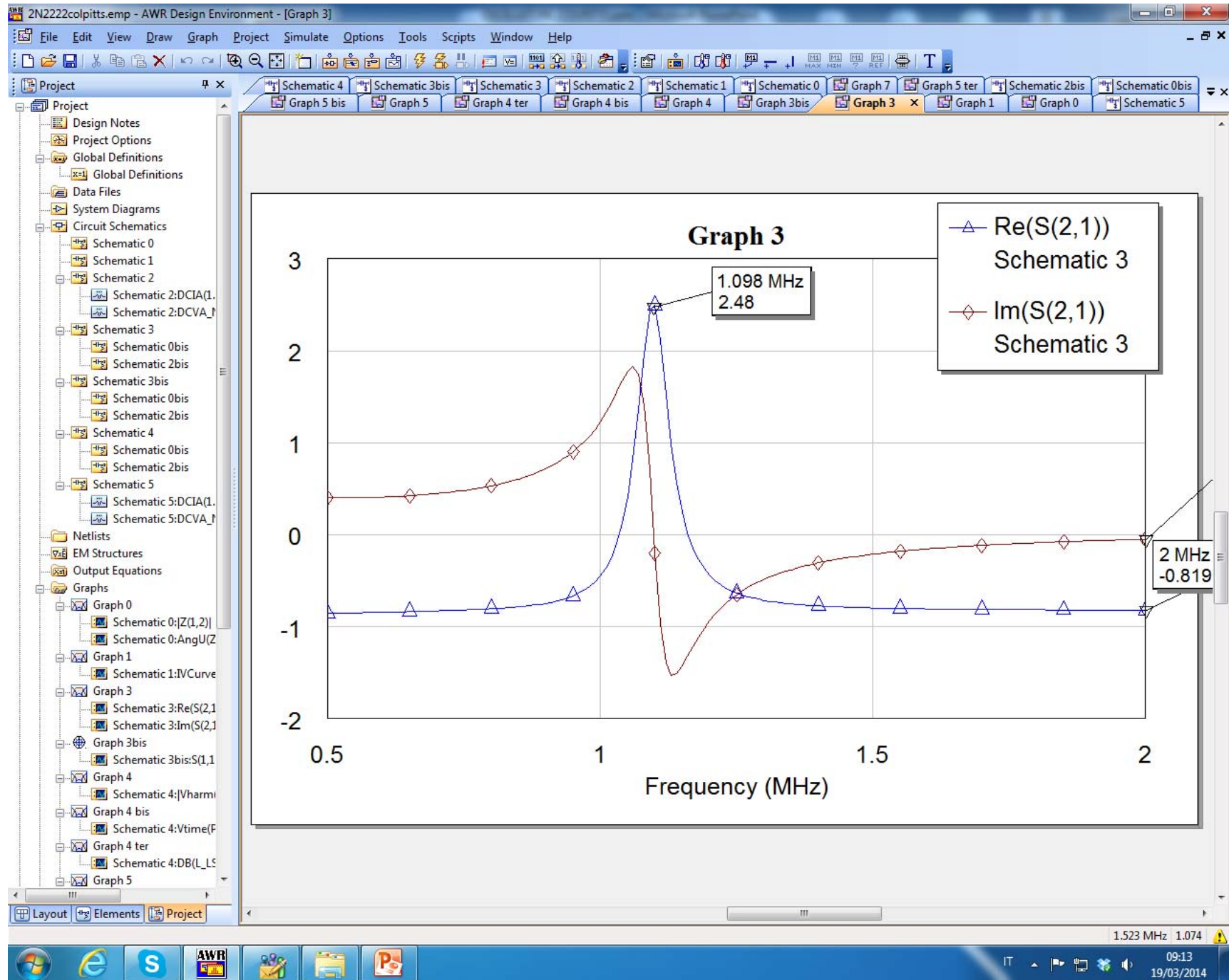

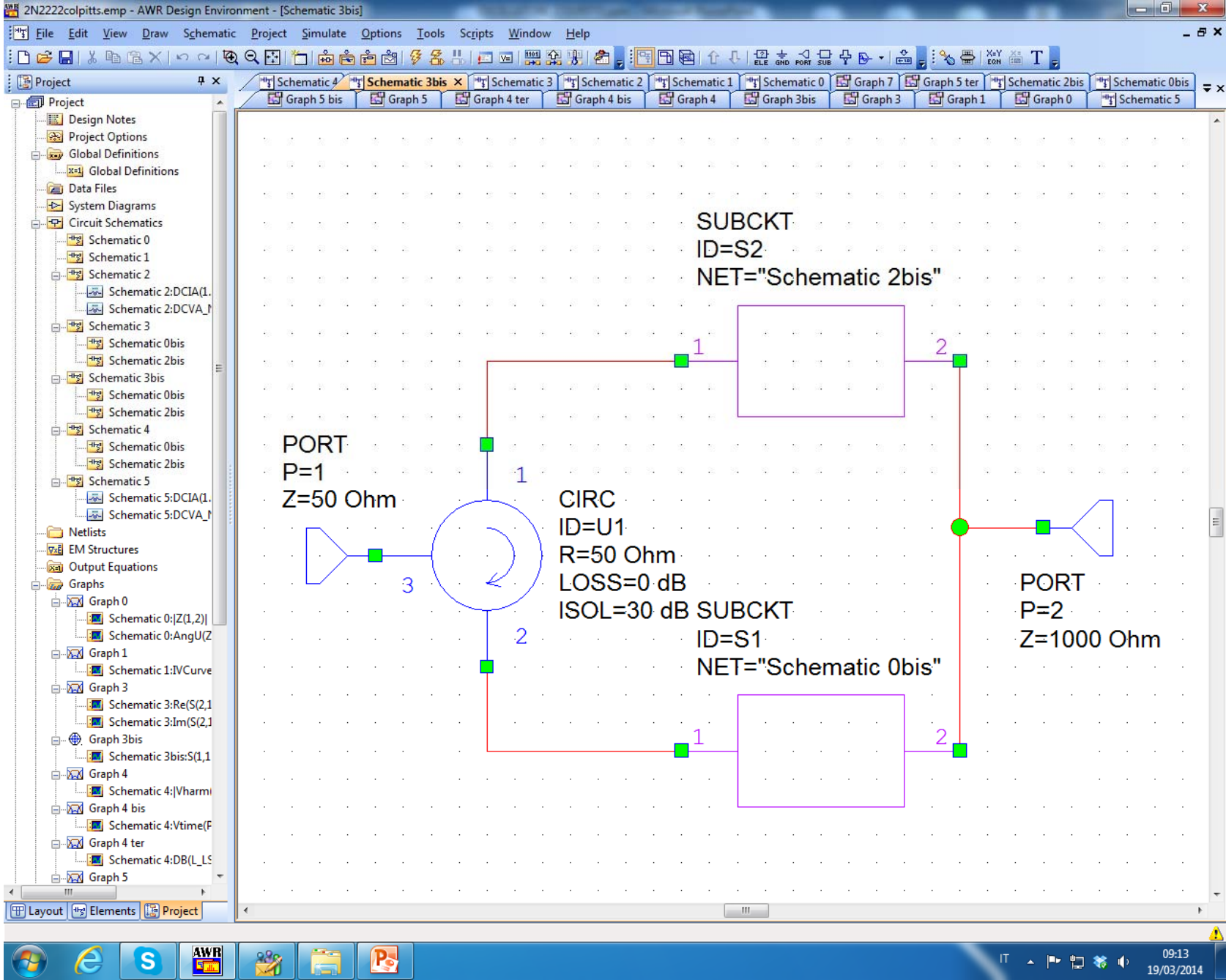

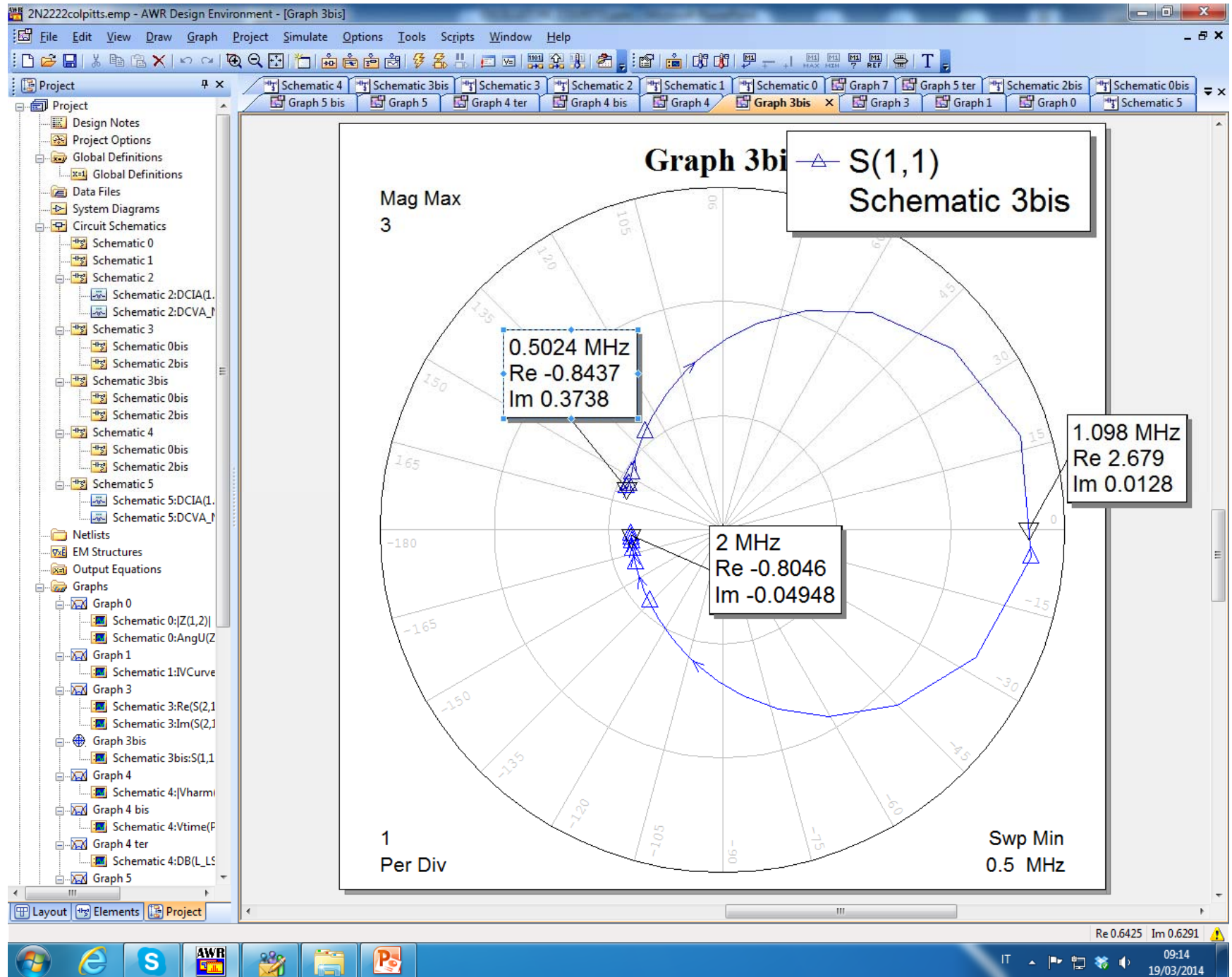

2N2222colpitts.emp - AWR Design Environment - [Schematic 4]

File Edit View Draw Schematic Project Simulate Options Tools Scripts Window Help

Project

- Design Notes
- Project Options
- Global Definitions
 - Global Definitions
- Data Files
- System Diagrams
- Circuit Schematics
 - Schematic 0
 - Schematic 1
 - Schematic 2
 - Schematic 2:DCIA(1)
 - Schematic 2:DCVA_1
 - Schematic 3
 - Schematic 3bis
 - Schematic 3bis
 - Schematic 3bis
 - Schematic 3bis
 - Schematic 4
 - Schematic 4bis
 - Schematic 4bis
 - Schematic 5
 - Schematic 5:DCIA(1)
 - Schematic 5:DCVA_1
- Netlists
- EM Structures
- Output Equations
- Graphs
 - Graph 0
 - Schematic 0:|Z(1,2)|
 - Schematic 0:AngU(Z)
 - Graph 1
 - Schematic 1:IVCurve
 - Graph 3
 - Schematic 3:Re(S(2,1))
 - Schematic 3:Im(S(2,1))
 - Graph 3bis
 - Schematic 3bis:S(1,1)
 - Graph 4
 - Schematic 4:|Vharm|
 - Graph 4 bis
 - Schematic 4:Vtime(F)
 - Graph 4 ter
 - Schematic 4:DB(L_LS)
 - Graph 5



OSCAPROBE
ID=X1
Fstart=0 MHz
Fend=4 MHz
Fsteps=2000
Vsteps=400


SUBCKT
ID=S2
NET="Schematic 2bis"

OSCNOISE
ID=NS1
OFstart=0.001 MHz
OFend=1 MHz
OFsteps=5
SwpType=LOG
Harm={ 1,2 }
NoiseContribs=Disabled

SUBCKT
ID=S1
NET="Schematic 0bis"

PORT
P=1
Z=1000 Ohm

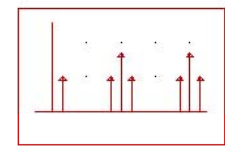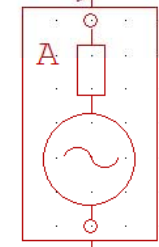

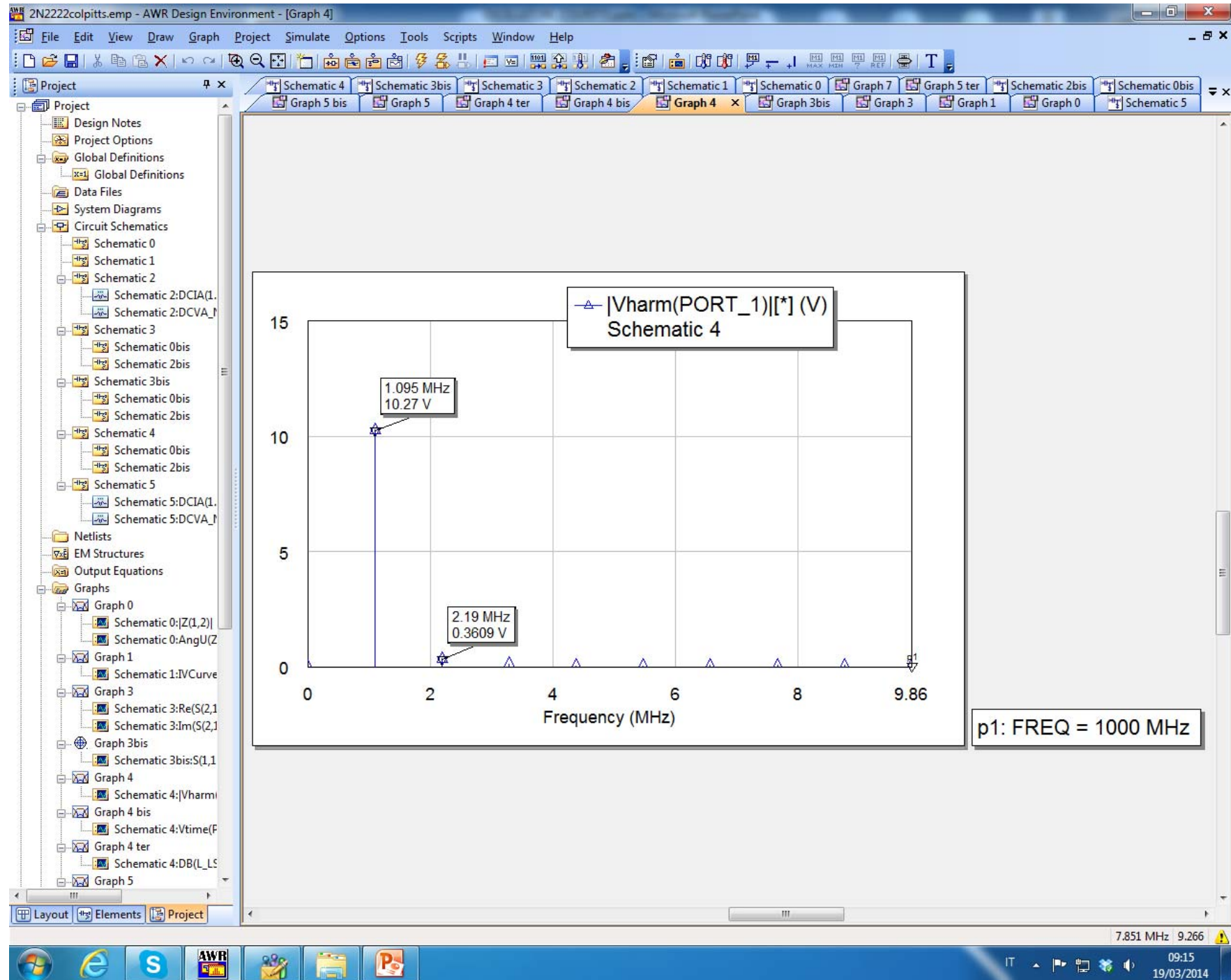

- Project
 - Design Notes
 - Project Options
 - Global Definitions
 - Global Definitions
 - Data Files
 - System Diagrams
 - Circuit Schematics
 - Schematic 0
 - Schematic 1
 - Schematic 2
 - Schematic 2:DCIA(1...
 - Schematic 2:DCVA_...
 - Schematic 3
 - Schematic 0bis
 - Schematic 2bis
 - Schematic 3bis
 - Schematic 0bis
 - Schematic 2bis
 - Schematic 4
 - Schematic 0bis
 - Schematic 2bis
 - Schematic 5
 - Schematic 5:DCIA(1...
 - Schematic 5:DCVA_...
 - Netlists
 - EM Structures
 - Output Equations
 - Graphs
 - Graph 0
 - Schematic 0:|Z(1,2)|
 - Schematic 0:AngU(Z
 - Graph 1
 - Schematic 1:IVCurve
 - Graph 3
 - Schematic 3:Re(S(2,1
 - Schematic 3:Im(S(2,1
 - Graph 3bis
 - Schematic 3bis:S(1,1
 - Graph 4
 - Schematic 4:|Vharm
 - Graph 4 bis
 - Schematic 4:Vtime(F
 - Graph 4 ter
 - Schematic 4:DB(L_LS
 - Graph 5

